



robocraze



[Home](#) [Post](#) [What is a Raindrop Sensor?](#)



What is a Raindrop Sensor?

On this page:

- [Summary](#)
- [Pin Configuration of Rain Drop Sensor](#)
- [Raindrop Sensor Features](#)
- [How to use the Raindrop Sensor](#)
- [Code:](#)
- [Rain Drop Sensor Working](#)
- [Applications](#)
- [Conclusion](#)
- [Frequently Asked Questions](#)

[See more](#)

[Share](#)



Reviews

Summary

As technology evolves, the use of sensor-based innovations in various fields has seen an incredible rise. Rainfall affects agriculture, water availability and hydropower generation - making it critical for us to understand how rain behaves. This is where a raindrop sensor comes into play. It allows us to measure rainfall with great accuracy and efficiency using advanced detection methods that provide real-time readings on changes in precipitation throughout a region or area. We will explore

what a raindrop sensor is, its types and some practical uses for this important piece of technology in this blog post. Let's get started!

The Raindrop sensors are used for the detection of rain and also for measuring rainfall intensity. Raindrop sensors can be used for all kinds of weather monitoring.

A raindrop sensor is a board on which nickel is coated in the form of lines. It works on the principle of resistance. The raindrop sensor measures the moisture via analog output pins and it provides a digital output when a threshold of moisture exceeds.

The module is based on the LM393 op amp. It consists of an electronics module and a printed circuit board that "collects" the rain drops. As raindrops are collected on the circuit board, they create paths of parallel resistance that are measured via the op-amp. It also has a power indicator LED and an adjustable sensitivity through a potentiometer.

Pin Configuration of Rain Drop Sensor

The raindrop control sensor is embedded with an LM393 voltage comparator, and current limiting resistors to adjust signal states and divide the voltage and capacitors as biasing elements.

The raindrop sensor control board is usually of the size 3.2cm x 1.4cm. The pin configuration is as detailed below:

VCC: This is the positive power supply pin that powers the sensor.

GND: This is the reference potential pin.

D0: This is the digital output pin of the internal comparator circuit.

A0: This is the analog output pin that gives analog signals between 0-5 Volts.

+/-: This is where the rain pad is connected to the LM393.

Raindrop Sensor Features

1. The LM393 uses a wide voltage comparator.
2. The sensor provides both digital and analog output.
3. It has an output LED indicator.
4. It is compatible with Arduino.
5. It is TTL Compatible.



6. The sensor uses the high-quality FR – 04 double material, a large area of 5.5 * 4.0 CM
7. Treatment of nickel plating and surface, has fight oxidation, electrical conductivity, and life has more superior performance.
8. The comparator output, signal clean, good waveform, and driving ability is strong, for more than 15 mA.
9. It has a potentiometer sensitivity adjustment.
10. The output format: digital switch output (0 and 1) and analog AO voltage output.
11. It has a fixed bolt hole, which is convenient for installation.
12. Adopts high-quality of RF-04 double-sided material.


How to use the Raindrop Sensor

We can interface it with Arduino. To do so we need the following components:

- Arduino Board
- Rain sensor module
- Pin connectors
- USB cable

Make the following connections:

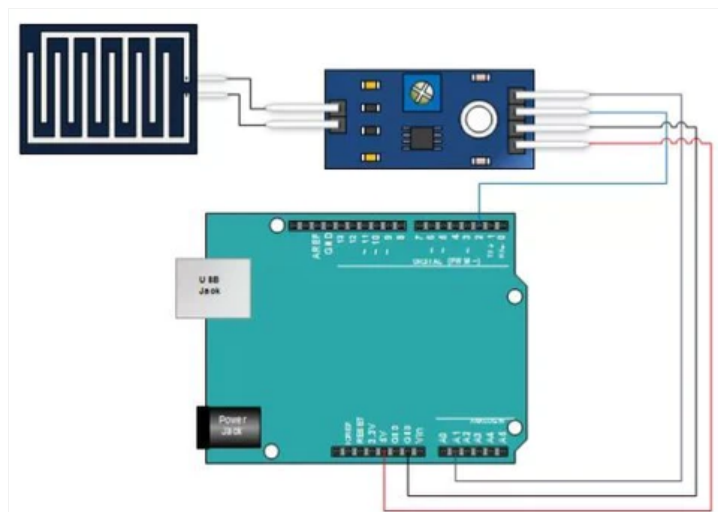- Raindrop Black Board +ve to the Integrated Chip +ve
- Raindrop Black Board –ve to the Integrated Chip –ve
- Vcc with Arduino Board +5V
- GND with Arduino Board GND
- Integrated Chip D0 with Arduino Board Digital pin 2
- Integrated Chip A0 with Arduino Board Analog pin A1



Raindrop sensor connected to an Arduino Uno

Use the above circuit as a reference for the connections.

Procedure:

1. Connect the components based on the figure shown in the wiring diagram and the instructions given earlier using pin connectors. The pin number will be based on the actual program code.
2. After the hardware connection, insert the sample sketch into the Arduino IDE.
3. Using a USB cable, connect the ports from the Arduino to the computer.
4. Upload the program.
5. See the results in the serial monitor

Code:

```
void setup()

{

// put your setup code here, to run once:

  Serial.begin (9600);

  pinMode (2 , INPUT);

}

void loop()

{

// put your main code here, to run repeatedly:

  int value = analogRead(A1);

  int digital = digitalRead(2);

  Serial.println (value);

  Serial.println (digital);

  delay(2000);
```



Reviews

```
}
```

Rain Drop Sensor Working

A raindrop sensor has a board on which nickel is coated in the form of lines. It works on the principle of resistance. The principle is that when there is no rain drop on board, the resistance is high so we get high voltage according to $V=IR$. When raindrops are present the resistance is reduced as water is a conductor of electricity and its presence connects nickel lines in parallel so the reduced resistance and there is a voltage drop across it.

Copper Pads

The working of the raindrop sensor module is easy and straightforward. The sensor has a series of exposed copper paths that act as variable resistors whose resistance varies according to the amount of water on its surface. Generally, they are not connected but are bridged through the water. This resistance is inversely proportional to the amount of water. The more water on the surface of the rain pads the better the conductivity and this results in lower resistance. The sensor produces an output voltage which is used to determine whether it is raining or not.

Sensor Module

The raindrop sensor module consists of a control sensor and a rain-sensing pad which can be connected to any microcontroller. The module produces an output voltage according to the resistance of the sensing pad and is given at the analog output pin. The same signal is also passed over to the LM393 high-precision comparator to digitize and is made available at the TTL digital output pin.

Control Circuit

In addition, the raindrop module has a potentiometer that is responsible for adjusting the output of the digital pin. This potentiometer is calibrated to receive accurate readings. The potentiometer is connected to the inverting end of the LM393 comparator and sets the reference or threshold voltage meanwhile the input analog voltage is applied to the non-inverting side of the comparator. Then the respective comparator compares both the voltages. This leads to two conditions and gives the output accordingly. If the voltage given as an input is more than the reference voltage then the comparator shows a high state.

Indication LED

Whereas if the threshold voltage is more than the applied voltage then the comparator output will be low. Apart from these, the module has two LEDs, a power LED and a status LED. The power LED will light up when the module is powered and the status LED glows and indicates the digital output pin status.

★
Reviews

Applications

The following are a few applications of raindrop sensors:

- It is used as a water preservation device and this is connected to the [irrigation system](#) to shut down the system in the event of rainfall.
- It is used to support the regular windscreen wiper's mode and to protect the internal parts of an automobile.
- This sensor is used in specialized satellite communications aerals for controlling and activating a rain blower over the opening of the aerial feed, to get rid of water droplets from the mylar wrap to keep pressurized as well as dry air within the waveguides.

Conclusion

In this blog post, we have learnt that the Raindrop Sensor is a versatile and efficient tool for measuring rainfall. With its simple PIN configuration and easy-to-use features, it provides accurate readings and offers a wide range of applications in fields such as agriculture, weather monitoring, and more. Whether you're looking to automate your irrigation system or monitor weather conditions for scientific purposes, the raindrop sensor provides reliable and accurate results. So have a [raindrop sensor](#) now and unlock the mysteries of precipitation!

If you appreciate our work don't forget to share this post and leave your opinion in the comment box.

Please do check out other [blog posts about Popular electronics](#)

Make sure you check out our wide range of [products and collections](#) (we offer some exciting deals!)



Reviews

Frequently Asked Questions

1. HOW DOES RAIN DROP SENSOR WORK?

Raindrop sensors utilise a conductive metal or a metallic layer that discerns the arrival of rain through electrical conductivity fluctuations. As raindrops shower down on the surface, they forge a conductive bridge, enabling an electric current to surge and be apprehended by the sensor, thereby

inciting a reaction, such as activating wipers or deactivating irrigation systems.

2. WHAT ARE THE APPLICATIONS OF RAIN DROP SENSOR?

Raindrop Sensors are employed in a plethora of usage scenarios, ranging from monitoring meteorological conditions to regulating irrigation, conserving H2O to delving into climatic investigations. They possess the ability to gauge precipitation quantities and furnish instant data, thereby enabling modification of irrigation setups, observing alterations in atmospheric phenomena and alleviating the plight of water scarcity.

3. HOW IS RAIN DETECTED?

Rain can be detected through various methods including radar, satellite imagery, and ground-based observation. Radars use radio waves to detect the presence and movement of precipitation, while satellites use infrared and visible light to observe and map the Earth's surface. Ground-based observation involves manual measurement of precipitation using instruments like rain gauges. These methods provide important data for weather forecasting and understanding of rainfall patterns.

[Back to blog](#)

Leave a comment




Reviews

Please note, comments need to be approved before they are published.

Post comment

Components and Supplies

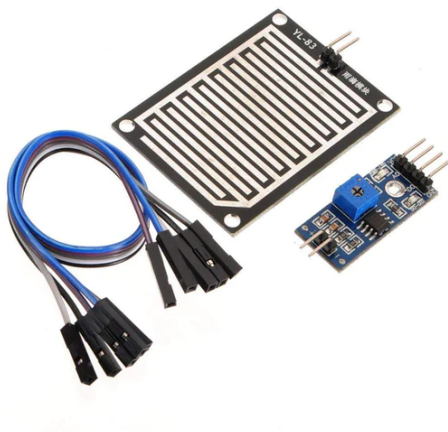

Rain Drop Sensor Module

★★★★★ 5

Rs. 73 Rs. 53

You save Rs. 20

Incl. GST (No Hidden Charges)

Add to cart

Buy it now



Arduino Uno Original with Cable

★★★★★ 19

Rs. 2,499 Rs. 2,199

You save Rs. 300

Incl. GST (No Hidden Charges)

Sold out

Buy it now

★
Reviews